



ugr | Universidad
de Granada

MOSFETS dosimetry

Miguel Ángel Carvajal Rodríguez

carvajal@ugr.es


ECsens, CITIC-UGR, Department of Electronics
University of Granada, E-18071 Granada, Spain

OUTLINE

- Introduction
- Radiation effects
- Constant current measurements
- Linear range improvement: Two currents method
- Thermal dependence:
 - Thermal model for lateral transistors
 - Thermal compensation: Three currents method
- Sensor module: Biased and unbiased modes
- Readout process: deferred mode
- Results and discussion


Introduction

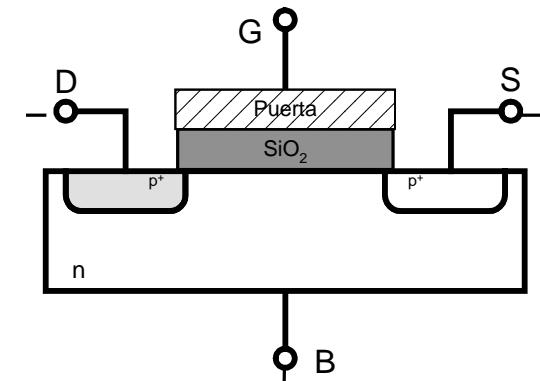- **Why MOSFET dosimeters for in-vivo dosimetry?**
 - Small size and low cost
 - Immediately readout
 - Linearity
 - Easy calibration
 - Reproducibility



Radiation effects

-

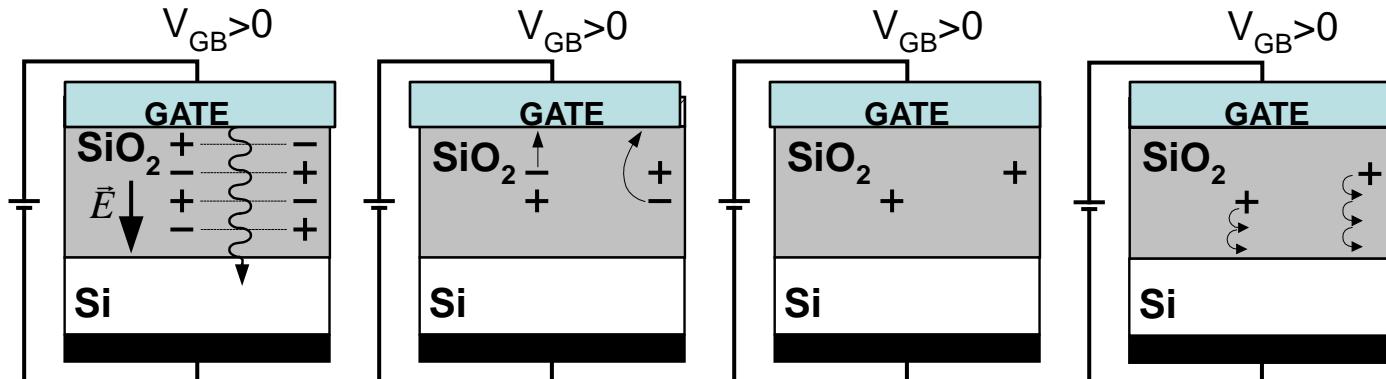


(a)

(b)

(c)


(d)

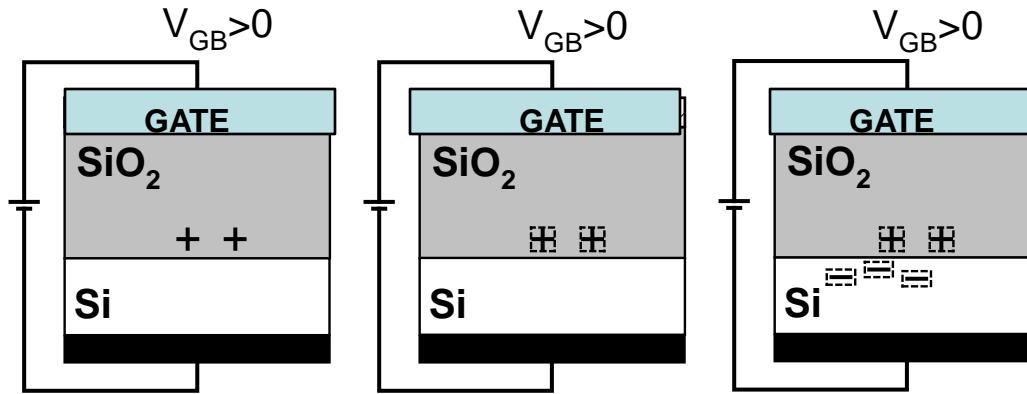

(e)

(f)



(g)

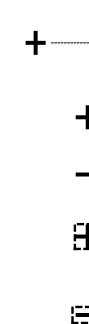
 + - Electron-hole pair
 + Hole
 - Electron
 ☐ Trapped hole
 ☐ Trap

Radiation effects

- Unbiased mode:
 - No external voltage.
 - Low sensitivity

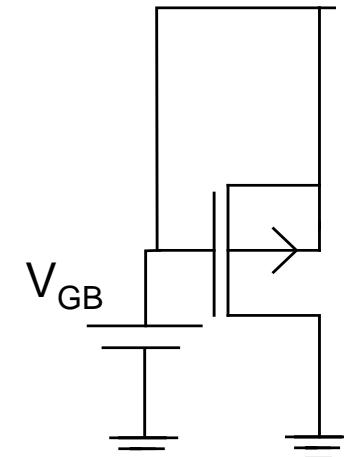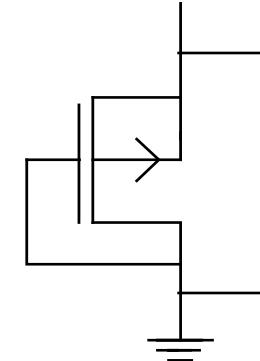
- Biased mode:
 - External V_{GB} during irradiation
 - Higher sensitivity and linearity.



Radiation effects

- Ionizing radiation creates charge in the oxide and traps in the Si-SiO₂ interface.
- Charge in oxide and positive traps produce an increment in the threshold voltage, |V_t|.
- Interface traps degrade the carriers mobility and then, the β parameter is reduced.

$$I_D = -\frac{\beta}{2} (|V_{GS}| - |V_t|)^2$$

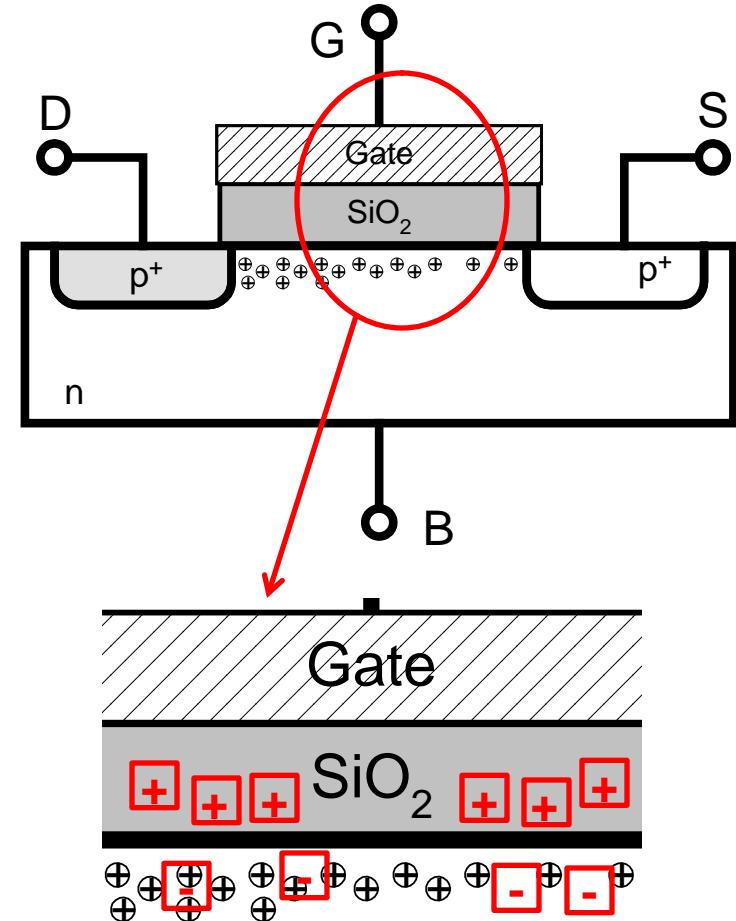

Constant current measurements

- Ionizing radiation creates charge in the oxide: Threshold voltage, V_t , is the dosimetric parameter


$$I_D = -\frac{\beta}{2} (|V_{GS}| - |V_t|)^2$$

$$\begin{aligned}\Delta/V_t &> 0 \\ \Delta\beta &< 0\end{aligned}$$

- Simplified measurement of V_t : V_S at constant drain current ($V_{GD} = 0$).


$$|V_t| = V_S - \sqrt{\frac{2I}{\beta}} \quad \beta \approx \text{constant} \Rightarrow$$

$$\Delta|V_t| \approx \Delta|V_S|$$

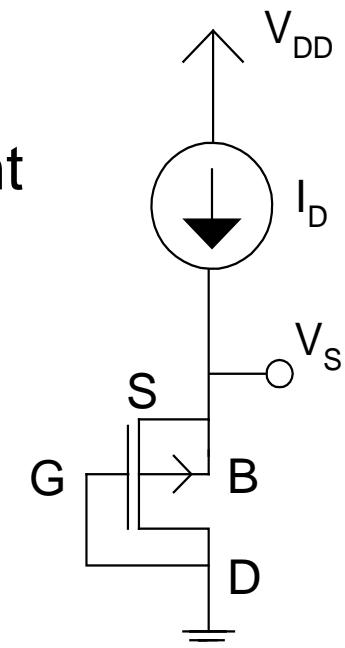

Radiation effects in electrical parameters

- | V_t | increases and β reduces with absorbed dose

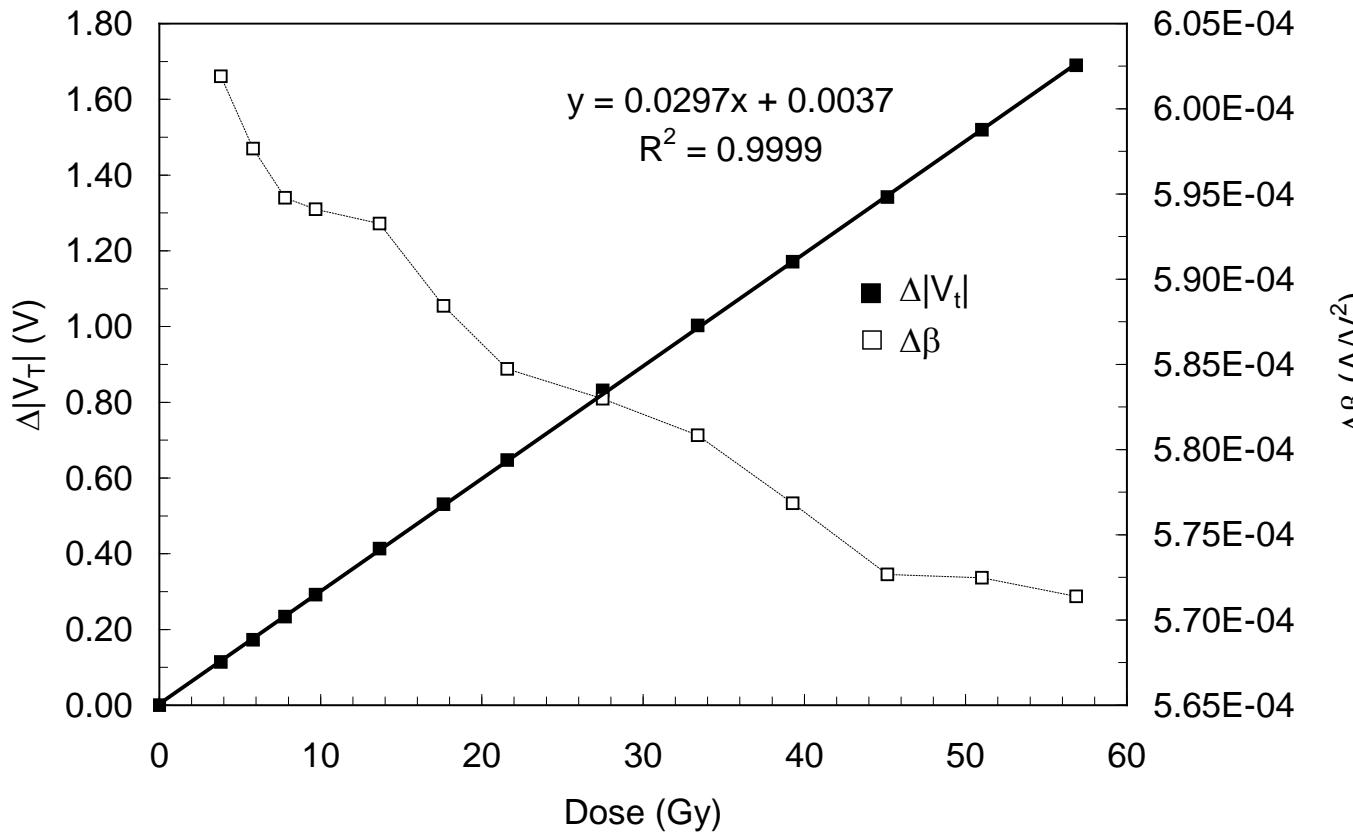

3N163, Vishay-Siliconix (USA)

- ^{60}Co Source
- Semiconductor analyser HP-4145B
- Unbiased mode

Linear range improvement: Two currents method (2CM)

- Accounting for $\Delta\beta$ effect in ΔV_t $I = \frac{\beta}{2} (V_s - |V_t|)^2$
- Pre- and post-irradiation parameters at constant current I :

$$|V_t| = V_s - \sqrt{\frac{2I}{\beta}} \Rightarrow \left\{ \begin{array}{l} |V_t^{post}| = V_s^{post} - \sqrt{\frac{2I}{\beta^{post}}} \\ |V_t^{pre}| = V_s^{pre} - \sqrt{\frac{2I}{\beta^{pre}}} \end{array} \right\} \quad \Delta|V_t| = \Delta V_s - \sqrt{2I} \left(\sqrt{\frac{1}{\beta^{post}}} - \sqrt{\frac{1}{\beta^{pre}}} \right)$$

Linear range improvement: Two currents method (2CM)

- Using two drain currents during read-out phase:

$$\Delta|V_t| = \Delta V_{S1} - \sqrt{2I_1} \left(\sqrt{\frac{1}{\beta^{post}}} - \sqrt{\frac{1}{\beta^{pre}}} \right) \quad \Delta|V_t| = \Delta V_{S2} - \sqrt{2I_2} \left(\sqrt{\frac{1}{\beta^{post}}} - \sqrt{\frac{1}{\beta^{pre}}} \right)$$

- Threshold voltage shift without neglecting β degradation

$$\boxed{\Delta|V_t| = \Delta V_{S1} + \frac{\Delta V_{S2} - \Delta V_{S1}}{1 - \sqrt{\frac{I_2}{I_1}}}}$$

- Problem:** Thermal compensated source voltage at two different currents are needed, thus the thermal compensation must be made using the thermal coefficient of V_t .

Thermal dependence


- Both $|V_t|$ and β decrease with temperature.

$$I_D = -\frac{\beta}{2} (|V_{GS}| - |V_t|)^2$$


↓

$$V_S = \sqrt{\frac{2|I_D|}{\beta}} + |V_t|$$

- Therefore, at constant current:
 - If $T \uparrow \rightarrow |V_t| \downarrow \rightarrow V_S \downarrow$
 - If $T \uparrow \rightarrow \beta \downarrow \rightarrow V_S \uparrow$

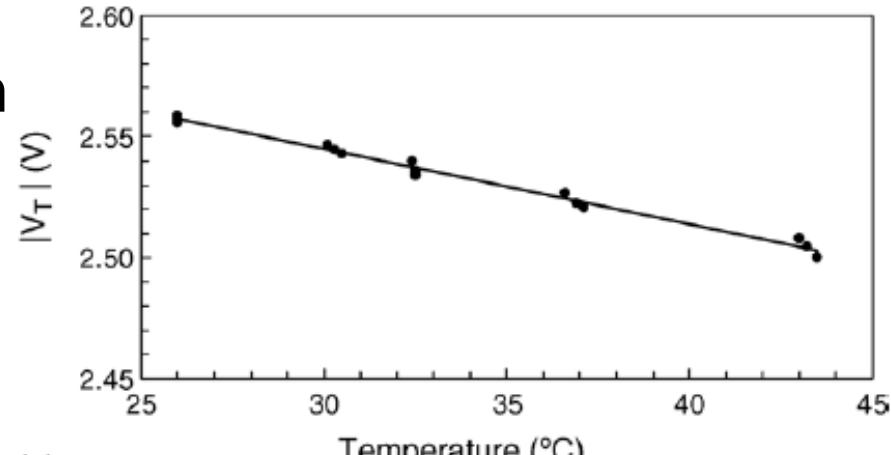

(a)


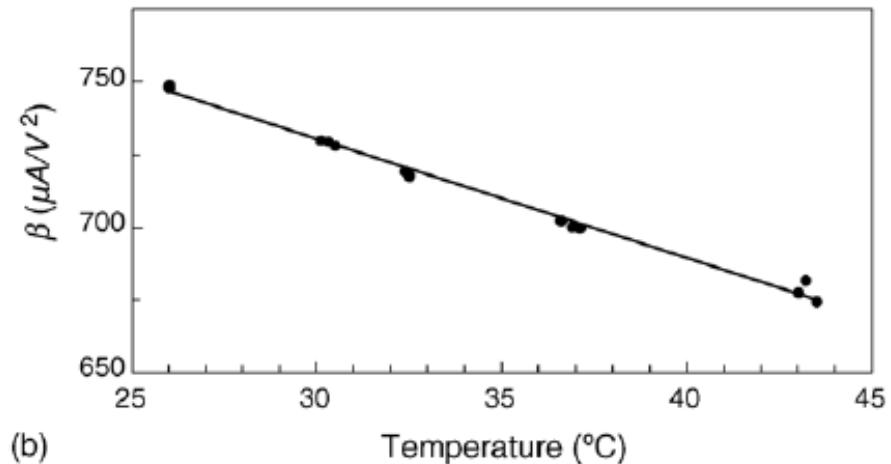


(b)

L.J. Asensio et al. / Sensors and Actuators A 125 (2006) 288–295

Thermal dependence

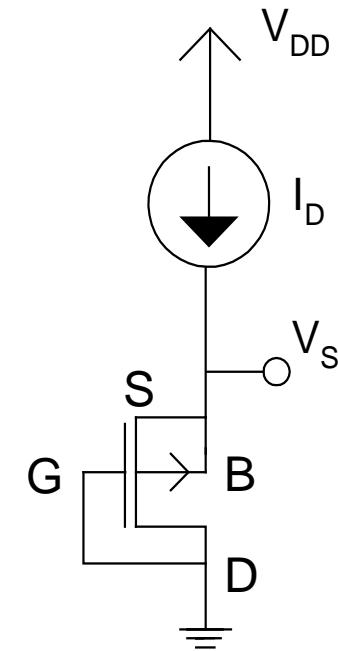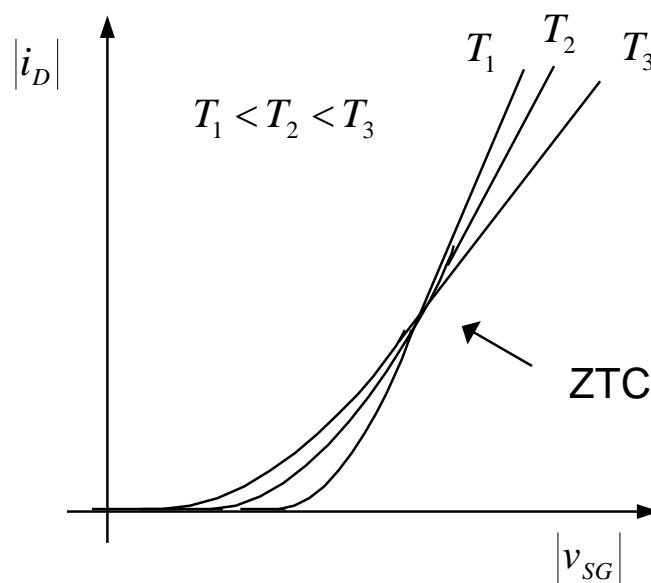- Both effects are compensated at I_{ZTC} current (Zero Temperature Coefficient)
- The thermal dependence of V_S is minimized at I_{ZTC} current



Thermal model for lateral transistors

- **Thermal compensation: Model**
 - Starting hypothesis: linear thermal trend of voltages

$$\left. \begin{array}{l}
 \Delta|V_t| = \Delta V_{S1} + \frac{\Delta V_{S2} - \Delta V_{S1}}{1 - \sqrt{\frac{I_2}{I_1}}} \\
 \Delta V_{S1} = \Delta V_{S1}^0 + \alpha_1 \Delta T \\
 \Delta V_{S2} = \Delta V_{S2}^0 + \alpha_2 \Delta T \\
 \Delta|V_t| = \Delta|V_t^0| + \alpha_{|Vt|} \Delta T
 \end{array} \right\} \Rightarrow \boxed{\alpha_i = \alpha_{|Vt|} \left(1 - \sqrt{\frac{I_i}{I_{ZTC}}} \right)}$$

Thermal compensation: Three currents method (3CM)

- **ΔV_S Thermal compensation: Adding a new current**

If no radiation: $\Delta V_{S1}^0 \approx \Delta V_{SC}^0$


$$\Delta V_{S1}(T) = \Delta V_{S1}^0 + \alpha_1 \Delta T$$

$$\Delta V_{SC}(T) = \Delta V_{SC}^0 + \alpha_C \Delta T$$

$$\Delta T \approx \frac{\Delta V_{S1} - \Delta V_{SC}}{\alpha_1 - \alpha_C}$$

$$\alpha = \alpha_{|V_t|} \left(1 - \sqrt{\frac{I}{I_{ZTC}}} \right)$$
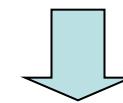
$$\Delta V_{S1}^0 = \Delta V_{S1} + \frac{\Delta V_{SC} - \Delta V_{S1}}{1 - \frac{\alpha_C}{\alpha_1}}$$



$$\boxed{\Delta V_{S1}^0 = \Delta V_{S1} + (\Delta V_{SC} - \Delta V_{S1}) \frac{\sqrt{I_1} - \sqrt{I_{ZTC}}}{\sqrt{I_1} - \sqrt{I_C}}}$$

PROCEDURES OF MEASUREMENT

Three currents method (3CM)

- **Thermal compensation**
 - $\Delta|V_t|$ thermal compensated

$$\Delta|V_t| = \Delta V_{S1}^0 + \frac{\Delta V_{S2}^0 - \Delta V_{S1}^0}{1 - \sqrt{\frac{I_2}{I_1}}}$$

- Simplification $I_1 = I_{ZTC}$

$$\Delta|V_t| = \Delta V_{S,ZTC} + \frac{\Delta V_{S2}^0 - \Delta V_{S,ZTC}}{1 - \sqrt{\frac{I_2}{I_{ZTC}}}}$$


- Additional current: I_C

$$\Delta V_{S2}^0 = \Delta V_{S2} + (\Delta V_{SC} - \Delta V_{S2}) \frac{\sqrt{I_2} - \sqrt{I_{ZTC}}}{\sqrt{I_2} - \sqrt{I_C}}$$

Thermal compensation: Three currents method (3CM)


- Thermal model:** Experimental validation (I)

3N163#1

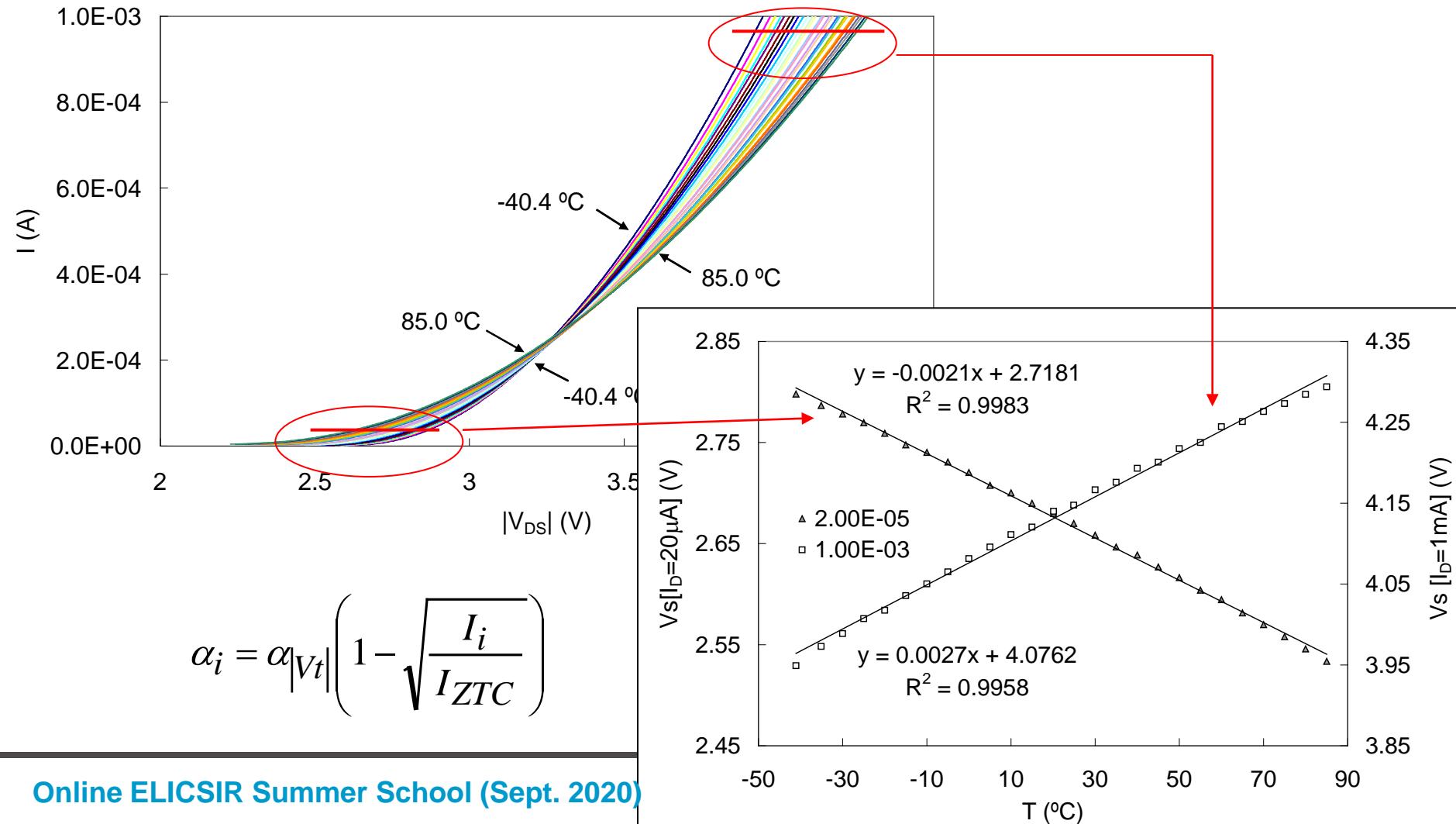

Thermal compensation: Three currents method (3CM)

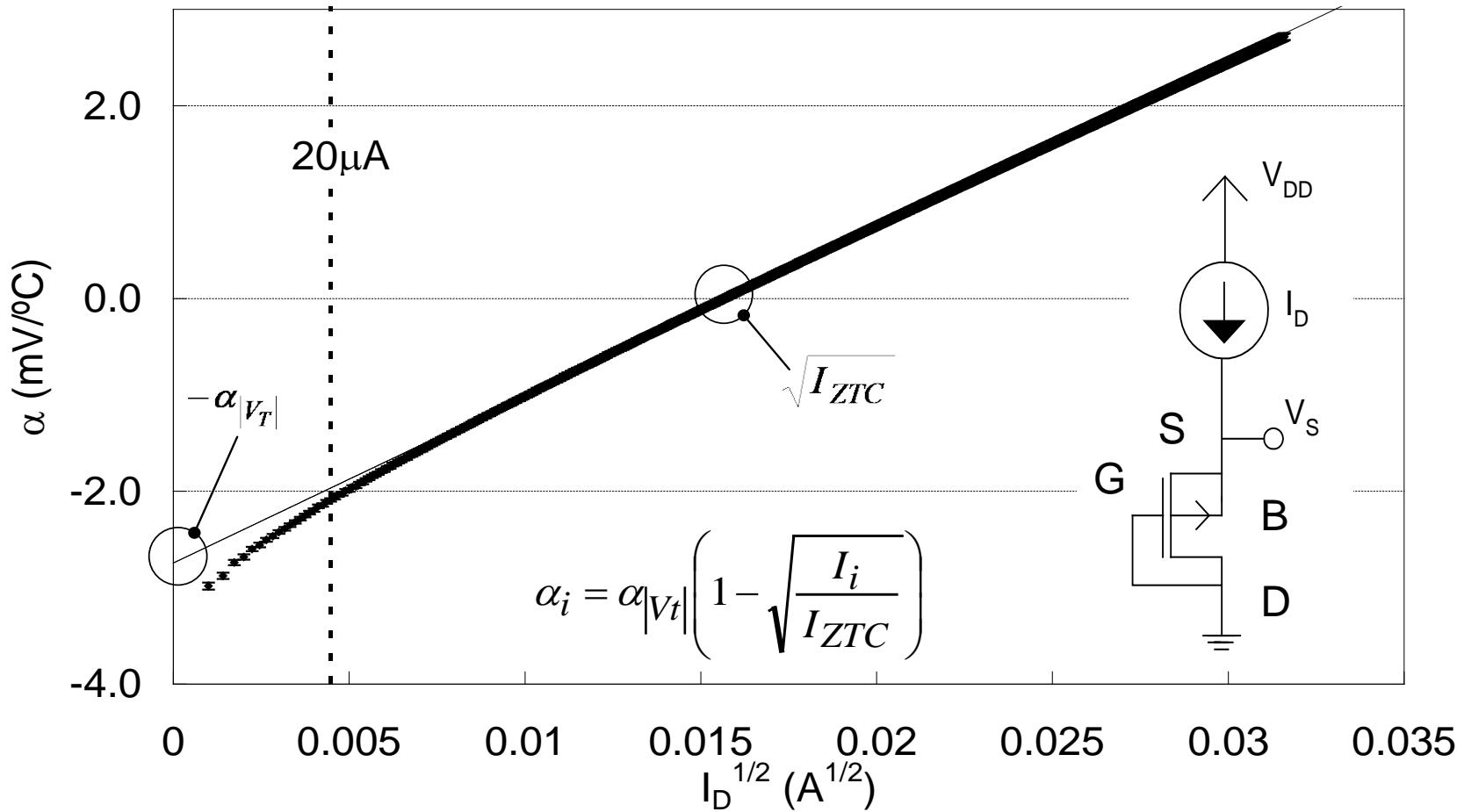
- **Thermal model:** Experimental verification (II)
3N163#1



Thermal compensation: Three currents method (3CM)

- **Thermal model:** Experimental verification (III)


CD4007#1

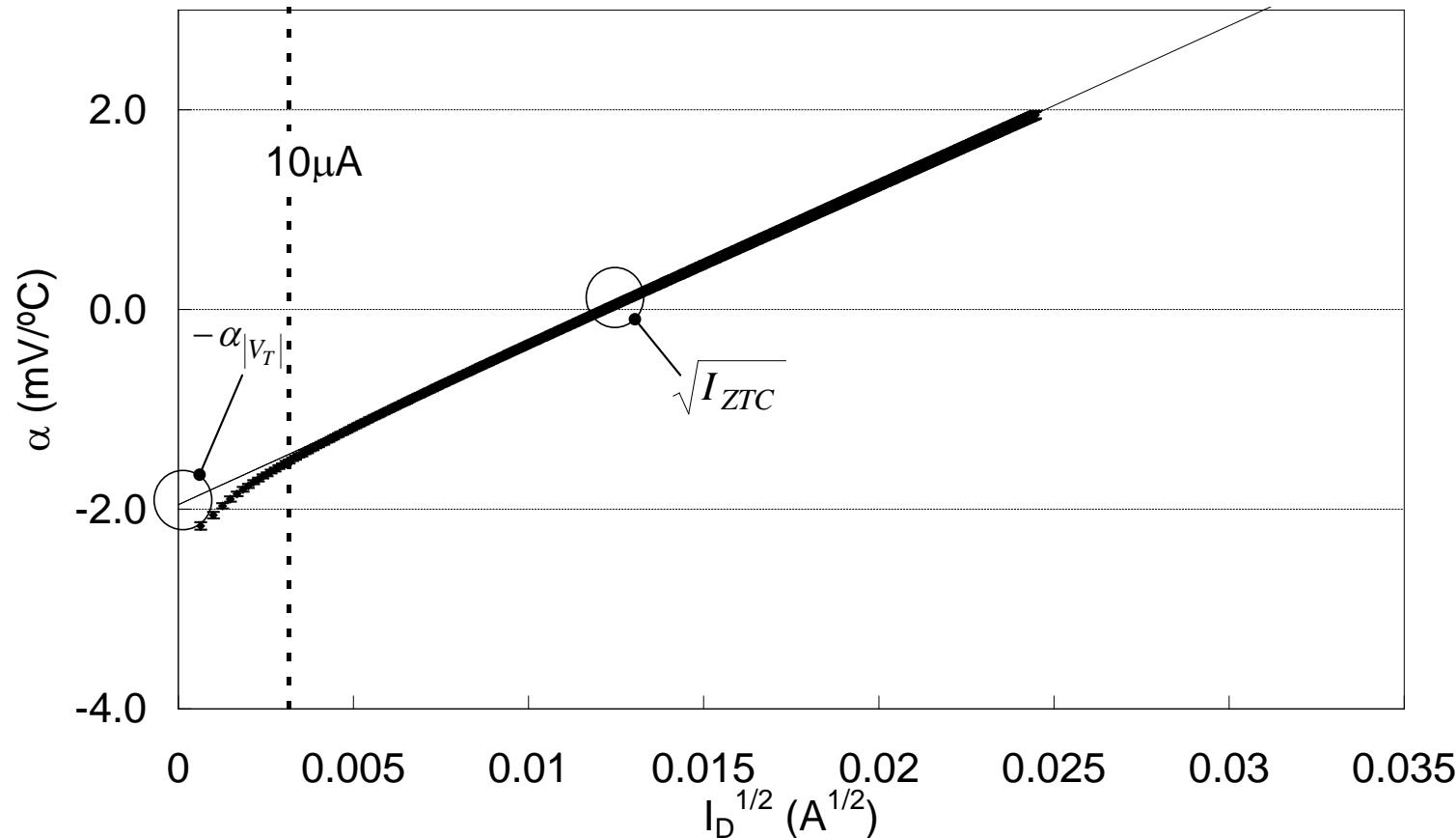

Thermal compensation: Three currents method (3CM)

- **Thermal model:** Experimental verification (IV)

RADFET 400nm#1

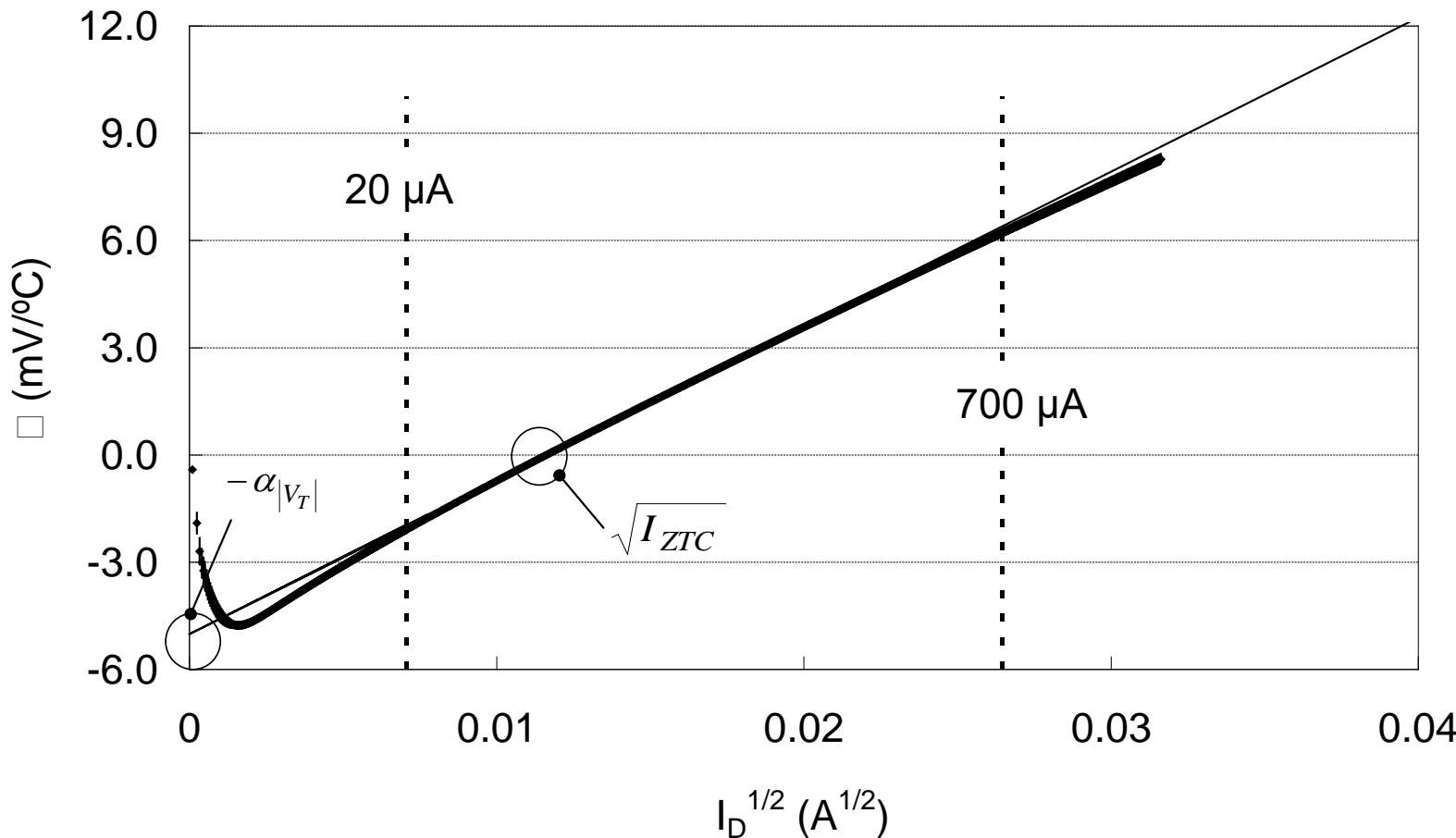

Thermal compensation: Three currents method (3CM)

- **Thermal model:** I_{ZTC} summary

$I_{ZTC}(\mu A)$ for lateral MOSFETs

| | Average | σ |
|--------------|---------|----------|
| 3N163 | 247 | 5 |
| CD4007 | 137 | 19 |
| RADFET 400nm | 136 | 6 |

Thermal compensation: Three currents method (3CM)

- **One current:**

- To thermal compensation $I_D = I_{ZTC}$. (usual mode)

- **Two currents:**

- To increase the linear range use $\Delta|V_t| = \Delta V_{S1} + \frac{\Delta V_{S2} - \Delta V_{S1}}{1 - \sqrt{\frac{I_2}{I_1}}}$
- To thermal compensation (without using I_{ZTC})

$$\Delta V_{S1}^0 = \Delta V_{S1} + (\Delta V_{SC} - \Delta V_{S1}) \frac{\sqrt{I_1} - \sqrt{I_{ZTC}}}{\sqrt{I_1} - \sqrt{I_C}}$$

- **Three currents:**


- Increasing the linear range and thermal compensation

$$\Delta V_{S2}^0 = \Delta V_{S2} + (\Delta V_{SC} - \Delta V_{S2}) \frac{\sqrt{I_2} - \sqrt{I_{ZTC}}}{\sqrt{I_2} - \sqrt{I_C}}$$


$$\Delta|V_t| = \Delta V_{S,ZTC} + \frac{\Delta V_{S2}^0 - \Delta V_{S,ZTC}}{1 - \sqrt{\frac{I_2}{I_{ZTC}}}}$$

Thermal compensation with two identical devices

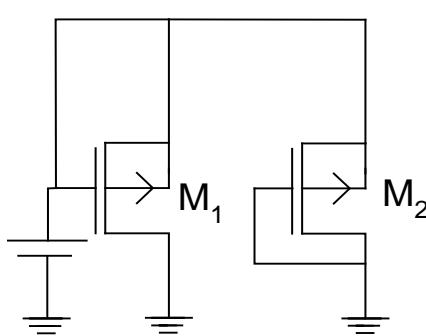- Sensing: Two identical pMOS with different sensibilities.
- Readout: Differential measurement.



During
irradiation

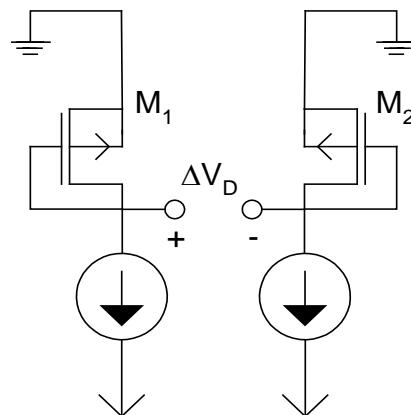


Read-out
configuration

Best medical canada



Thermal compensation using two identical devices

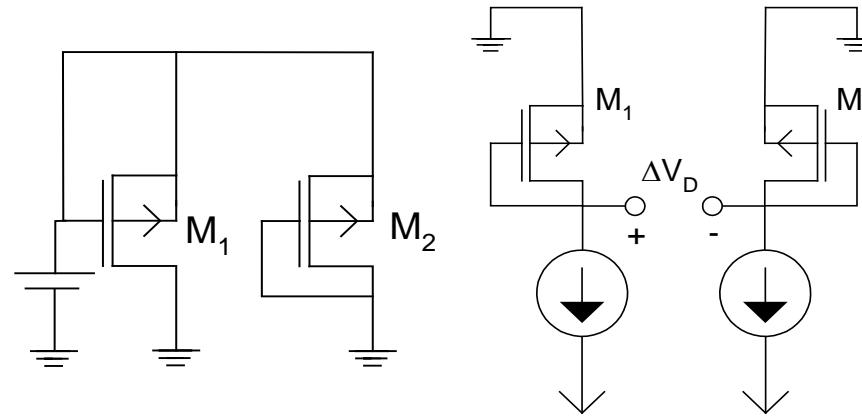- During irradiation: Two different bias voltage, therefore different sensitivity to radiation
- The readout is carried out with the same conditions minimizing the interference of the temperature.



During
irradiation

$$\left. \begin{array}{l} \Delta V_{S1} = S_1 D \\ \Delta V_{S2} = S_2 D \end{array} \right\} \Rightarrow \Delta V_D = (S_1 - S_2)D$$

Read-out
configuration

Thermal compensation techniques: Summary


- ONE TRANSISTOR (Lateral MOSFET):
 - One current: I_{ZTC} .
 - Two currents: Out of I_{ZTC} zone.
 - Three currents: I_{ZTC} and two currents for thermal compensation and linear range improvement.
- TWO TRANSISTORS:
 - Different bias voltages during irradiation and differential measurements.

PROCEDURES OF MEASUREMENT

Pulsed biasing (PB)

■ SNR improvement

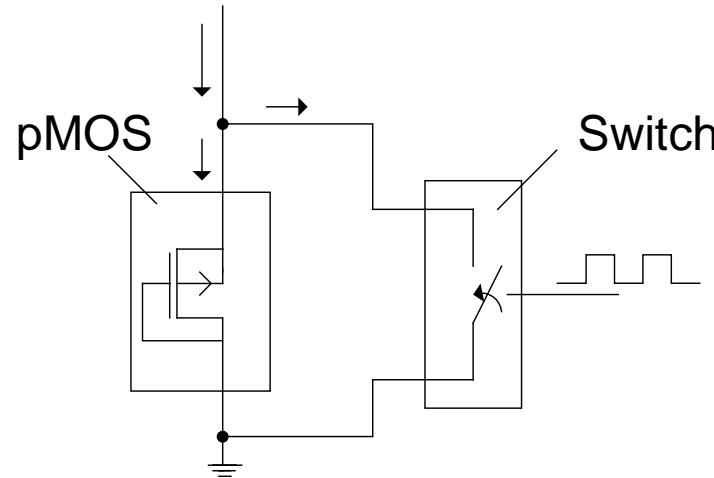
- Read-time instabilities caused by low frequency noise (LFN) (due to near-interface and interface traps)
- How can LFN be reduced? Chopping the drain current as in other experimental techniques (i.e. spectroscopy) and averaging




Sensor module

■ Unbiased mode

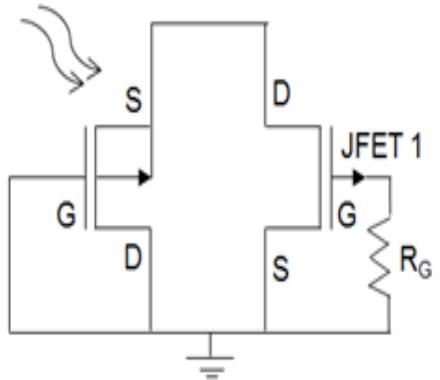
- JFET as a switch (shortcircuited during irradiation and storage and open during read-out)



Irradiation and storage

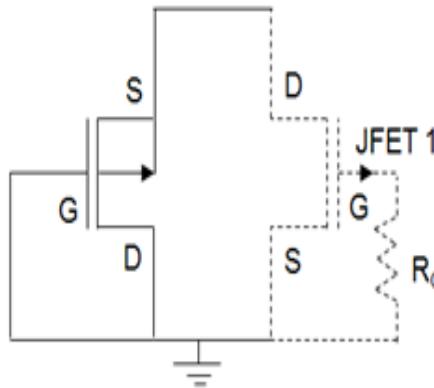




During readout

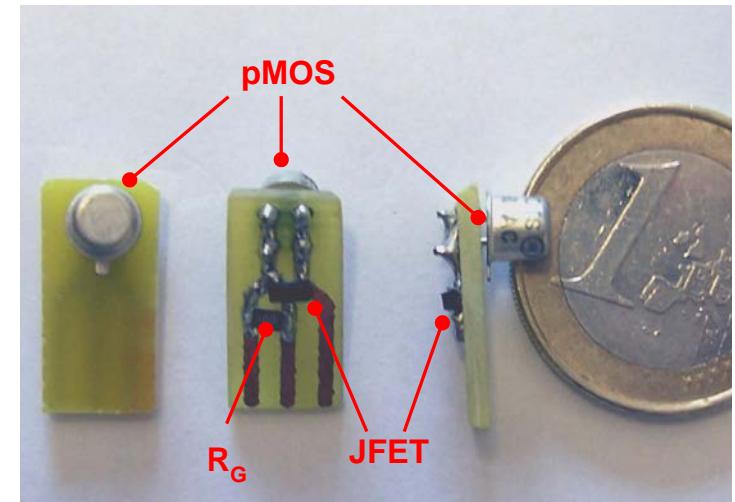


Sensor module

- **Biased mode:** Two JFET as switches

CD4007

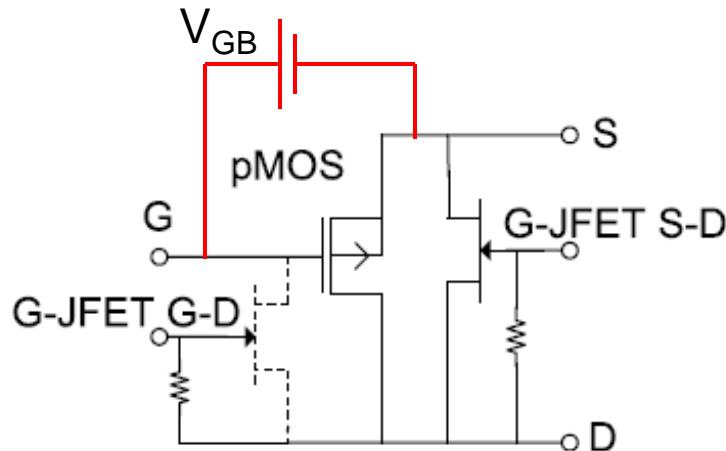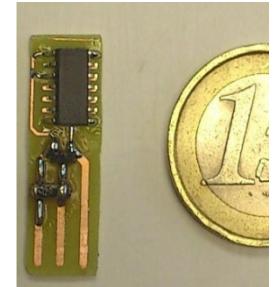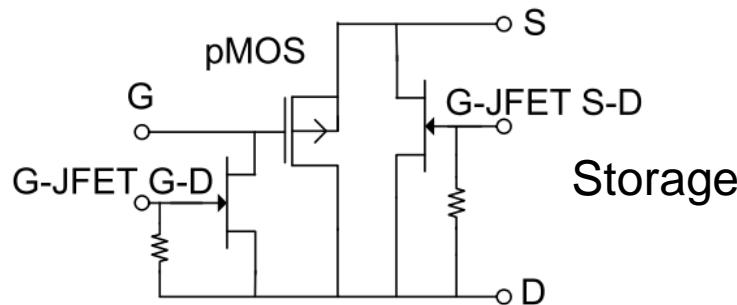


Irradiation

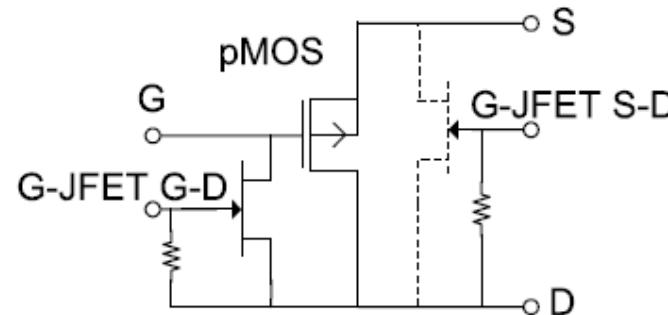

Readout

RADFET

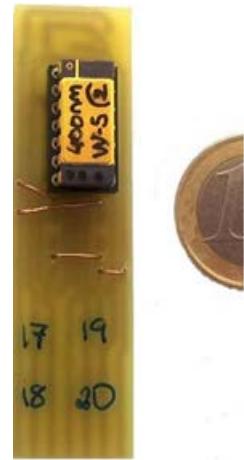

Readout process: deferred mode

Dose measurement process


- Zeroing:
 - Measurement and storage of pre-irradiation V_S at the two (three) drain currents
- Irradiation
- Timeout for short-term fading (2-3 minutes)
- Dose measurement
 - Recovery of the pre-irradiation values from the memory.
 - Measurement and storage of the post-irradiation V_S at the two (three) currents
 - Dose calculation (calibration is required)



Results for 3N163 (unbiased and deferred mode): (PB+2CM)

- Linearity improvement**

- Irradiation source: Siemens KDS-6MV.

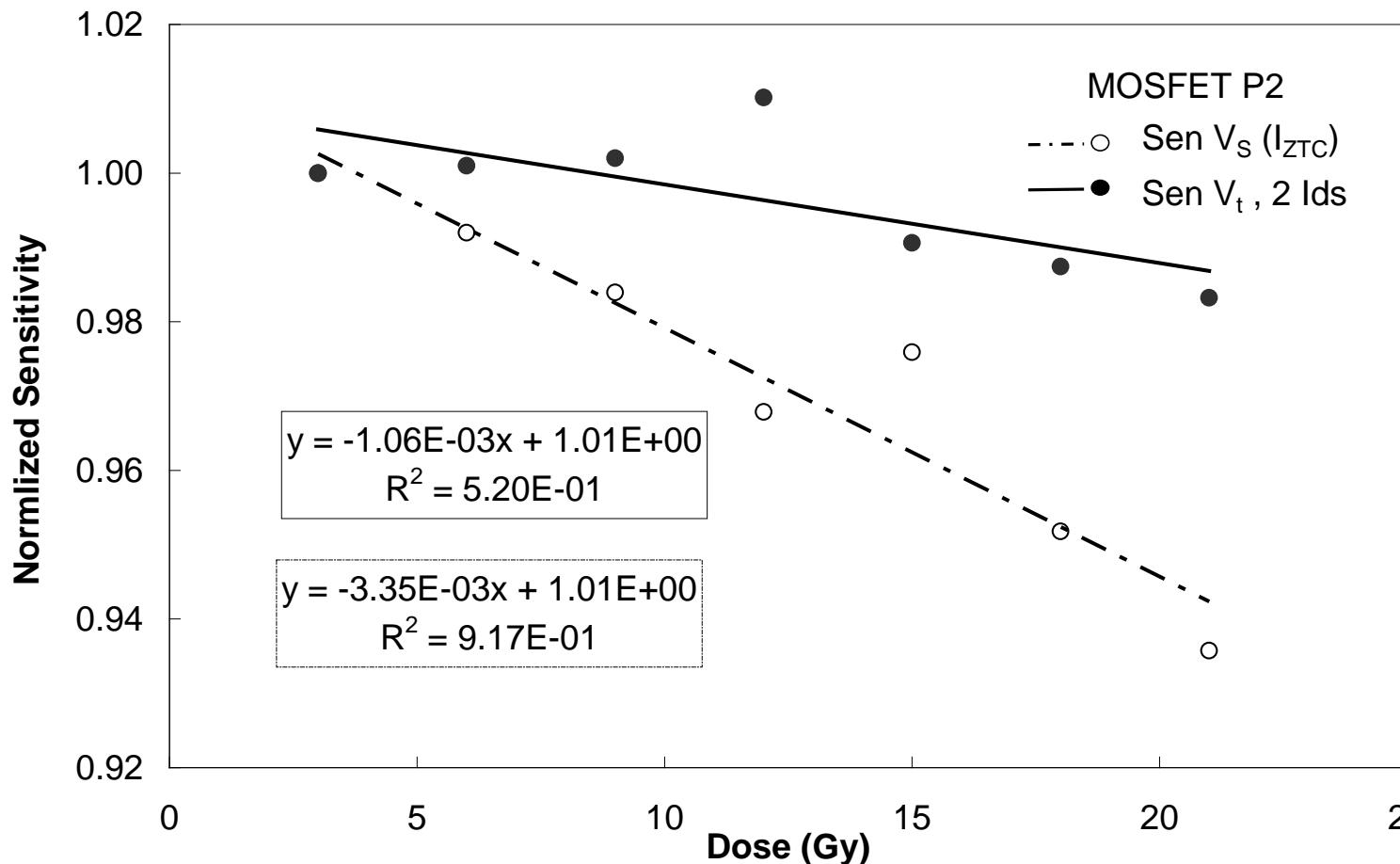

Results for 3N163 (unbiased and deferred mode): (PB+2CM)

■ Linearity improvement

- Sensitivity decay coefficient, mean sensitivity and the linear limit (up to 5%).

| | DC modes | | PB | |
|-----------------------------|------------|--------|-----------|-------------|
| | I_{ZTC} | 2CM | I_{ZTC} | 2CM |
| m (mV/Gy ²) | -0.153 | -0.095 | -0.113 | -0.057 |
| Mean Sensitivity (mV/Gy) | 20.6 | 19.7 | 20.0 | 19.2 |
| Linear Range (Gy) | 6.8 | 10.3 | 8.8 | 16.8 |

20 % reduction of SD

$$\sigma_{Vs}^{DC} = 45.8 \mu V$$

$$\sigma_{Vs}^{PB} = 36.4 \mu V$$

Experimental results for 3N163 (3CM)

- Thermal compensation:**

- Reduction in a factor of **50** in the thermal drift


$$I_2 = 30 \mu\text{A}$$

$$I_3 = 120 \mu\text{A}$$

$$I_{ZTC} = 247 \mu\text{A}$$


- Compensated
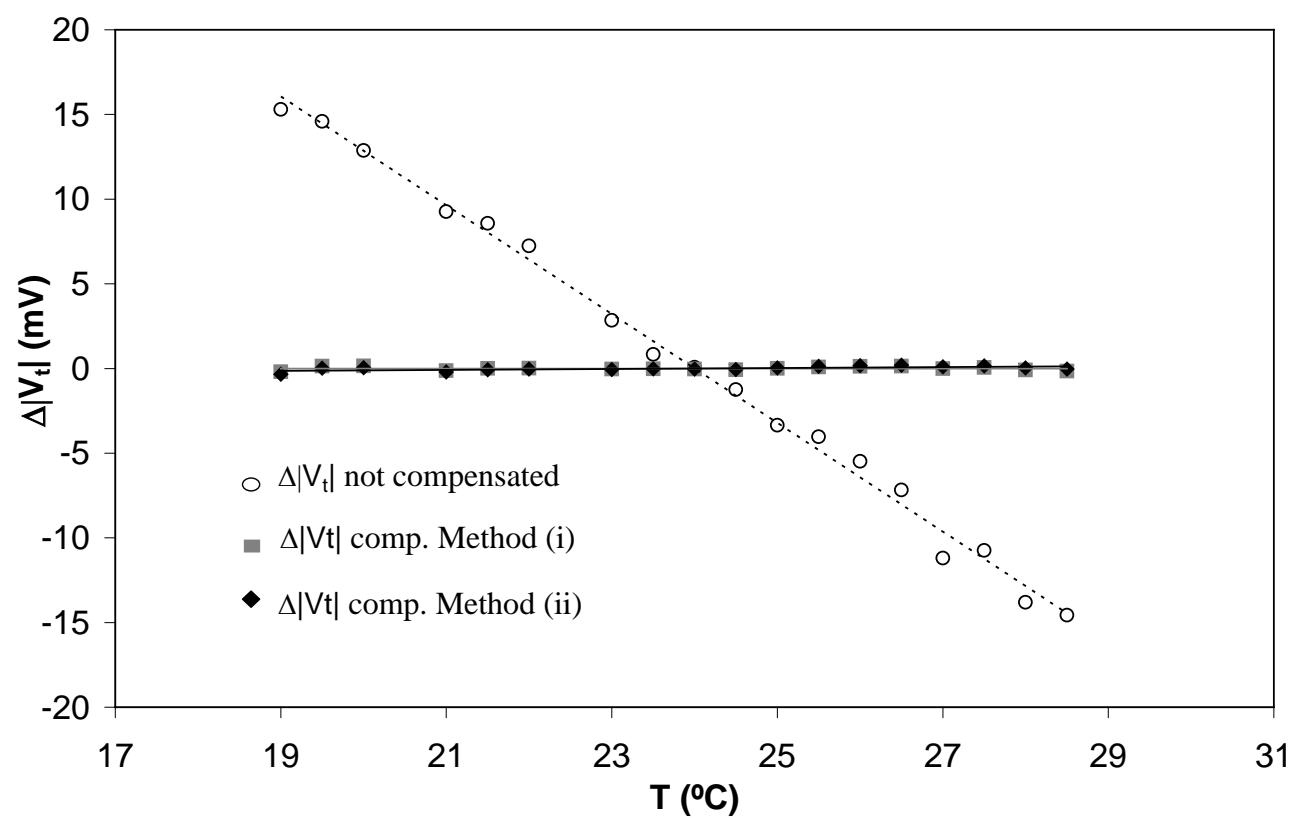
$$\frac{\Delta V_t}{\Delta T} < 70 \mu\text{V}/^\circ\text{C}$$



- Radiation response of 3N163

Dpre=30 Gy (^{60}Co)

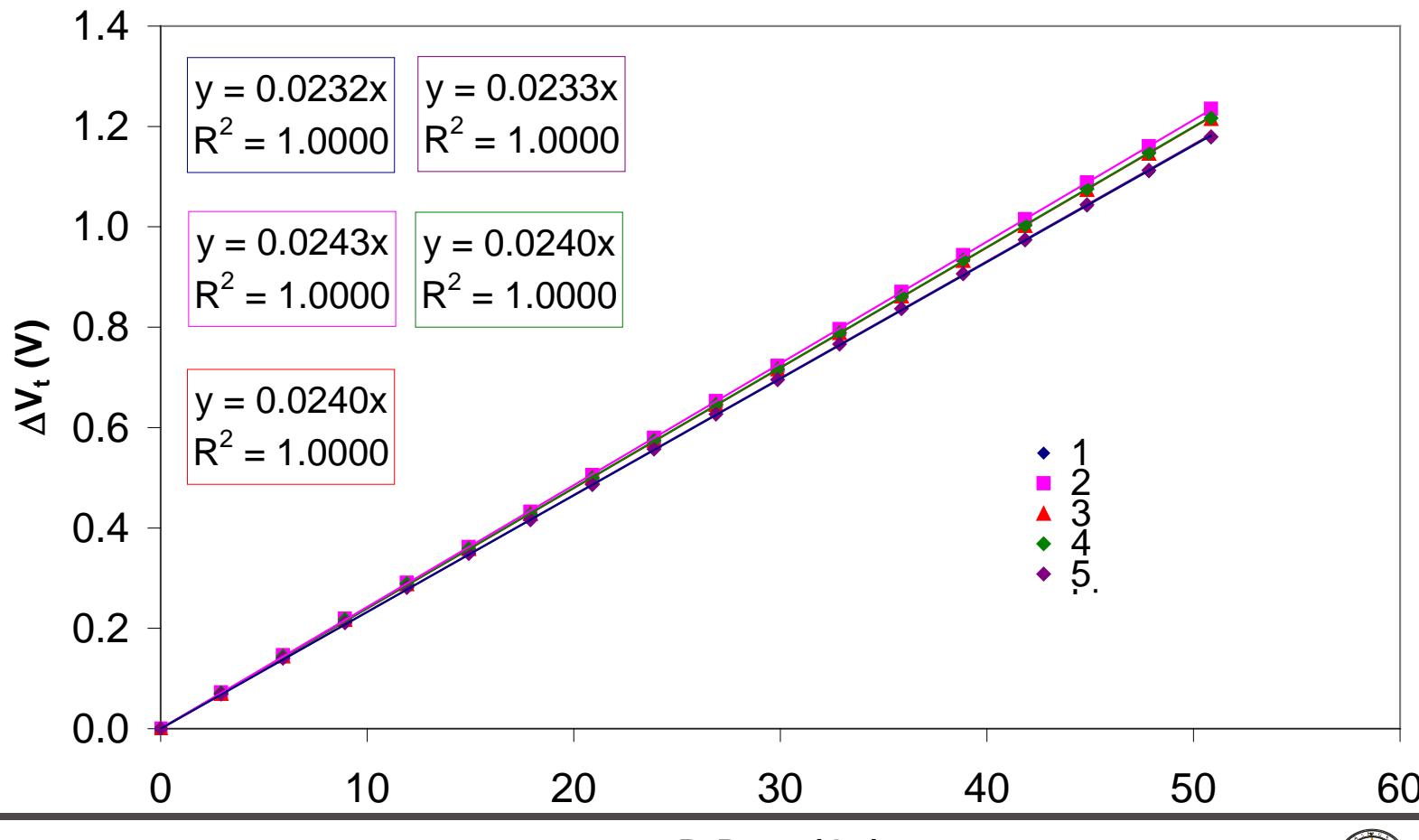


Unbiased and deferred mode (3CM+PB): 3N163

| | |
|-------------------------|--------------------|
| Temperature range | 10 – 40 °C |
| Resolution | 1 cGy |
| Accuracy | ± 3 % |
| Linear range | 15 Gy > 80 Gy * |
| Thermal drift | < 3mGy/°C |
| Delay after irradiation | 2 – 3 minutes |


* with recalibrations every 15 Gy

Note: For 3N163 transistor

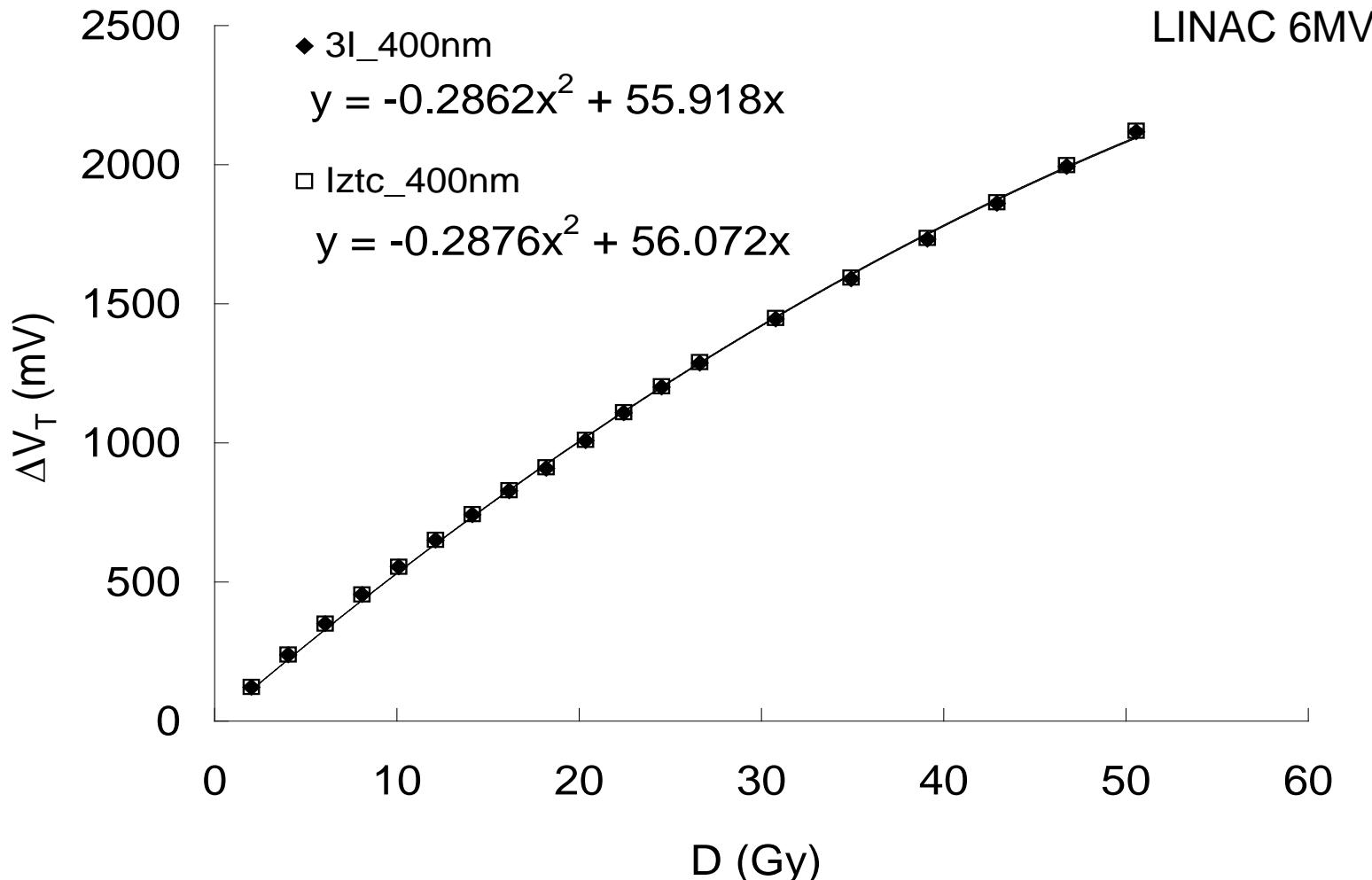Dosimetry characterization, results RADFET 400nm



Deferred mode (3CM+PB): Summary

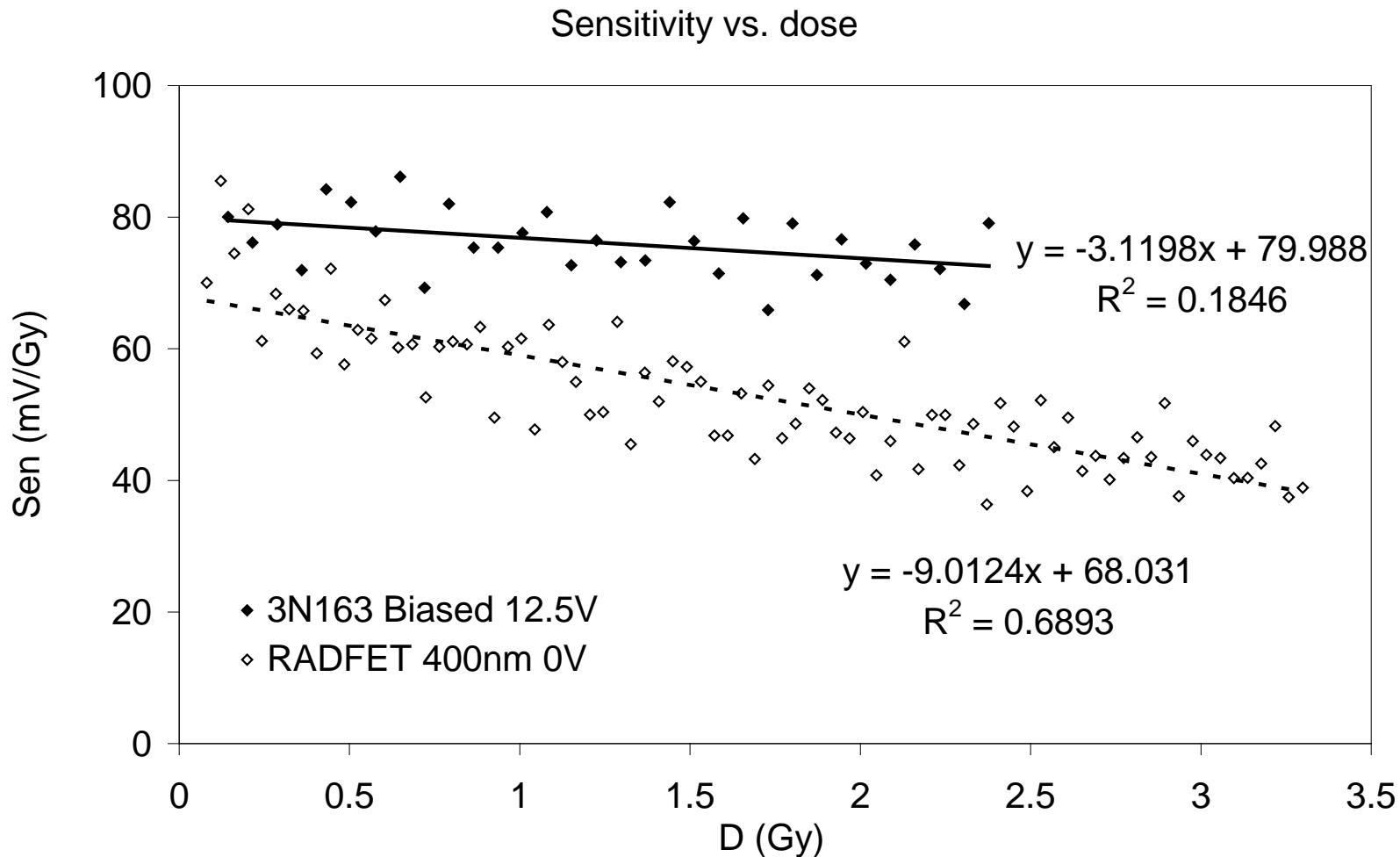

Deferred mode (3CM+PB): Summary

| | Sensitivity (mV/Gy) | Bias (V) |
|---------------|---------------------|----------|
| CD4007 | 5.24 ± 0.17 | 0 |
| 3N163 | 21.5 ± 1.1 | 0 |
| | 48 ± 3 | 5 |
| | 55 ± 3 | 10 |
| RADFET | 55.4 ± 1.2 | 0 |

- Thermal model has been applied to RADFETs and lateral commercial transistors
- For RADFETs 3CM and I_{ZTC} method are equivalent
- 3N163 biased at 10 V presents a sensitivity similar to RADFETs of 400 nm in unbiased model, but showing much more fading.

Future talks

- Internal topology of the reader unit will be described
 - Programmable current source
 - Hardware for zeroing and resolution improvement
- Real-time measurements
- DMOS transistor:
 - Thermal compensation
 - Additional hardware required
 - Radiation response
- Etc.

The background image shows a stunning sunset or sunrise over a vast expanse of low-hanging clouds. In the foreground, dark, silhouetted mountain peaks are visible. A bright sun sits on the horizon, casting a warm orange glow across the sky and reflecting off the tops of the clouds.

See you in Granada

It's
here!

Thank you for your attention

Miguel Ángel Carvajal Rodríguez
University of Granada (Spain)

carvajal@ugr.es